 


A **sub-nanosecond** time-resolved gating circuit


Kayla Rodriguez and Scarlett Yu
Department of Physics and Astronomy, UCLA

Dated: June 5th, 2018


Background story - system and objective





Background story - system and objective

 



Background story - system and objective

 


Background story - system and objective

  


Background story - system and objective

  

Unwanted spikes from laser pulses

 


Background story - system and objective

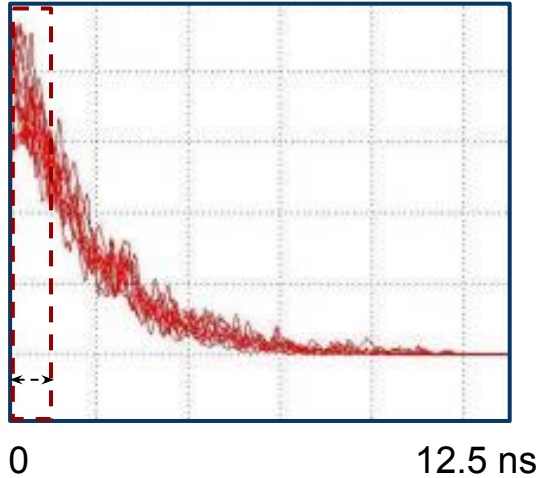


How to take out this pico-second signal?

Background story - system and objective

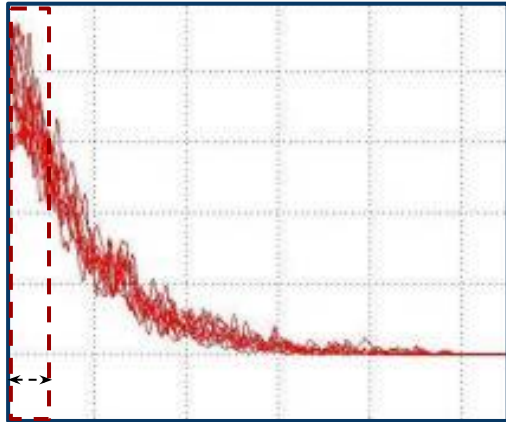

0 12.5 ns

How to take out this pico-second signal?

 


Picosec fast shutter?



Time tagging? \$\$\$


Search for Possible Approaches (Week 2)

 

Two routes:

- Time tag the arrival time of each photon.
 - Eg. Use **very** small (um) CMOS-based TDC (time-digital converter)
 - Eg. Subdivide the clock cycle in a TDC. But **low data storage and retrieval rate.**
- Some sort of gate

Search for Possible Approaches (Week 2)

 


Two routes:

- Time tag the arrival time of each photon.
 - Eg. Use **very** small (um) CMOS-based TDC (time-digital converter)
 - Eg. Subdivide the clock cycle in a TDC. But **low data storage and retrieval rate.**
- Some sort of gate




An analog solution:

Initial proposed logic

 


Starting out with lab parts (Week 3-4)

 

1. Delay: two BNC cables of different lengths
2. XOR gates: tried different types

Types	Model	T_{pd} (ns)
NANDS in lab	SNX4LS00	9
XORs in lab	CD4070B	6.8
Purchased XORs	7AC11086	3.8

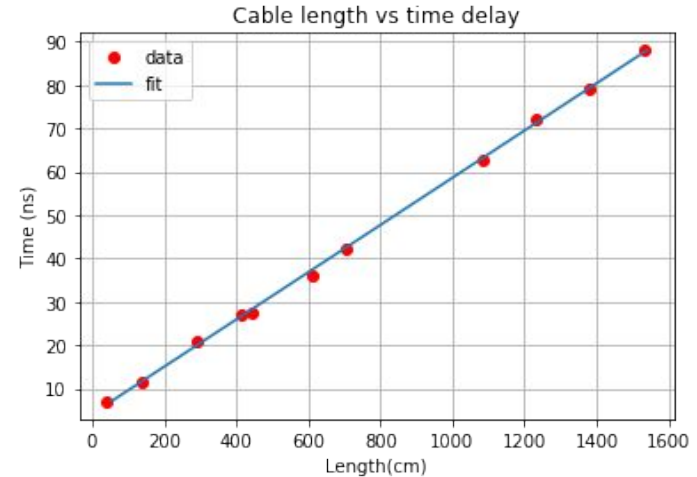

Time delay created $\Delta t \sim$ Difference in length ΔL



Beta versions - Result Summary (Week 3-4)

ver.	XOR type	Model	T_{pd} (ns)
0.9.1	NANDS in lab	SNX4LS00	9
0.9.2	XORs in lab	CD4070B	6.8
0.9.3	Purchased XORs	7AC11086	3.8


- Multiple stages, very slow.
- Output was noisy, unable to resolve the Δt delay

- Able to resolve hundreds of ns.
- Logic worked, but output not as desired.

  - Clean sq-wave output with 68ns Δt , but attenuated amplitude.




x1 attenuation

 



x10 attenuation

Beta versions - Final output (Week 5)

 

 
 
3. AND gate (from 117 lab)

- Made with fastest XOR gates
- *Rigol Waveform Generator*: simulate the PMT noise signal to check logic.




Main Problems & Design Modification (Week 5)

 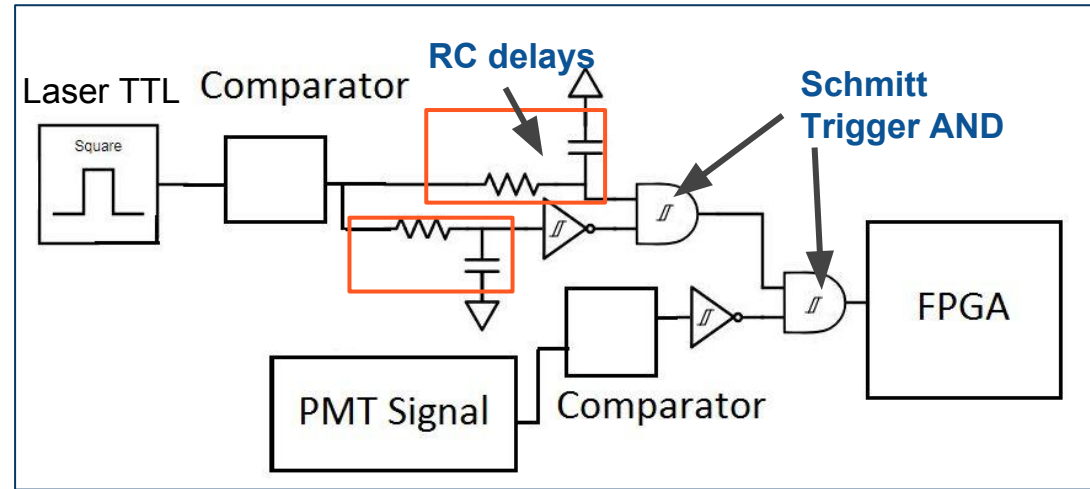
1. Output has 2x frequency than inputs?
 - XOR → AND w/ schmitt trigger on rising edges
2. New method of delay:
 - RC delay
3. Input amplitude (laser TTL) too low for gate operation?
 - Use comparators




XOR

 

AND

 


Improved versions and add-ons (Week 5-6)

 


Ver. 1.0

Improved versions and add-ons (Week 5-6)

 


Ver. 1.0

 


Ver. 2.0

- **Buffer gates:** take a signal that's trying real hard to be digital, clean it up and turn it into a nice, sharp TTL
- **Decoupling/bypass capacitors**
- **Impedance matching resistors**

Improved versions and add-ons (Week 5-6)

 


Ver. 1.0

 


Ver. 2.0

- **Buffer gates:** take a signal that's trying real hard to be digital, clean it up and turn it into a nice, sharp TTL
- **Decoupling/bypass capacitors**
- **Impedance matching resistors**

Improved versions and add-ons (Week 5-6)

 

Ver. 1.0

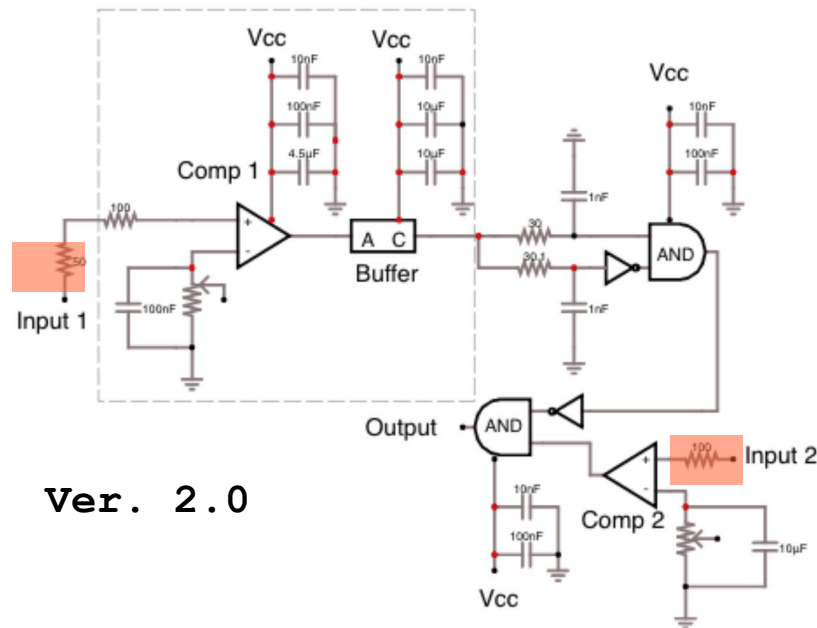

Ver. 2.0

- **Buffer gates:** take a signal that's trying real hard to be digital, clean it up and turn it into a nice, sharp TTL
- **Decoupling/bypass capacitors**
- **Impedance matching resistors**

High-speed PCB Design, and Printing (Week 6-8)

Issues to consider:

Timing. Signals on the PCB arriving at the proper time relative to each other?

Integrity. Signal waveforms the same at the final point as the starting point?


Noise. What kind of noise does the signal encounter during its journey on the board?


Solutions:

Impedance: Proper impedance between your transmitter and receiver.

Match lengths, account for propagation delay: Match lengths of two coupled traces s.t. signals arrive at the same time.

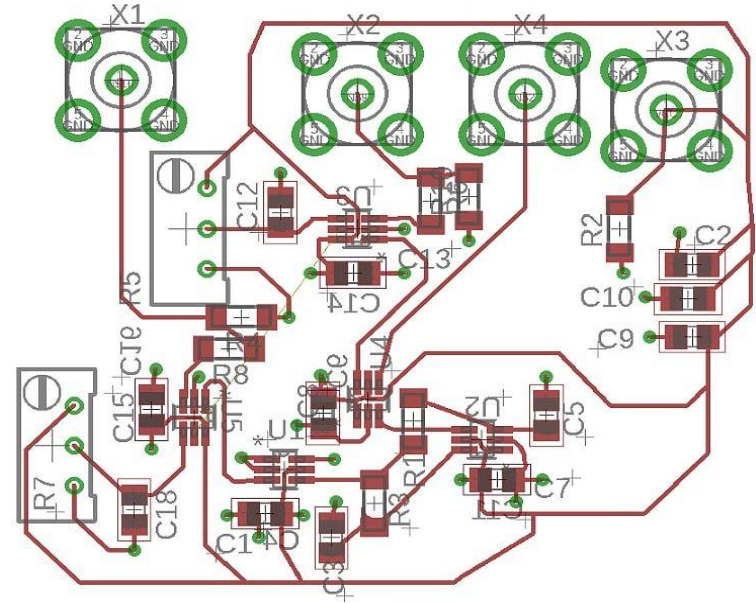
Spacing: Close traces are the more susceptible to noise and signal interference.



 

Soldering (Week 9) - a soul-refreshing learning experience

One mistake was made → manually reroute

 

- Keep temperature ~low
- Chip by chip, start from corner.
- Test each part as we solder.
- Be careful & patient...

Testing part by part (Week 10)

Systematically checked:


1. Power, all inputs
2. Inputs & outputs of the comparators
 - a. Tuned potentiometer
 - b. Tried with simple square wave
 - c. Tried with real signals
3. Inputs & Outputs of gates

“A failure will not appear till a unit has passed final inspection.”



Testing with real inputs (Week 10)



PMT

 

- Both signals go negative
- Noisy, has ringing


Laser

Tuning the pot to clean up

  

Newest problems and fixes (Week 10)

 - Made the wrong connections
 - Small wires to reroute
- Needed to include a voltage divider
 - Piling resistors
- Laser signal not stable when testing
 - impedance matching



Final Budget

Items	Quantity	Price
Boards	4	176.00
AND chips	15	4.17
SMAs	8	39.04
Comparators	12	50.28

Grand Total: \$269.49


Original Plan:

HMC721LC3C(FAST XOR GATE) from DigiKey. **\$150 each x 2**

Previous Plan: \$300.00

Acknowledgements & References

 - Christian, Tony for help w/ circuit design
- Peter Yu and Prof. Saltzberg for lending us cables and soldering tools.



[1] Cheng, Zeng, etc. *Recent Developments and Design Challenges of High-Performance Ring Oscillator*


[2] Porat, Dan I. *Review of sub-nanosecond Time-interval Measurements.*

[\[3\] Spetra-Physics Tsunami manual](#)

Testing with real inputs (Week 10)

Laser pulse monitor signal

 
- Amplitude too small for logic
- No offset, goes below 0V
- Impedance matching to keep the laser locked






END


THIS PAGE IS INTENTIONALLY LEFT BLANK

 

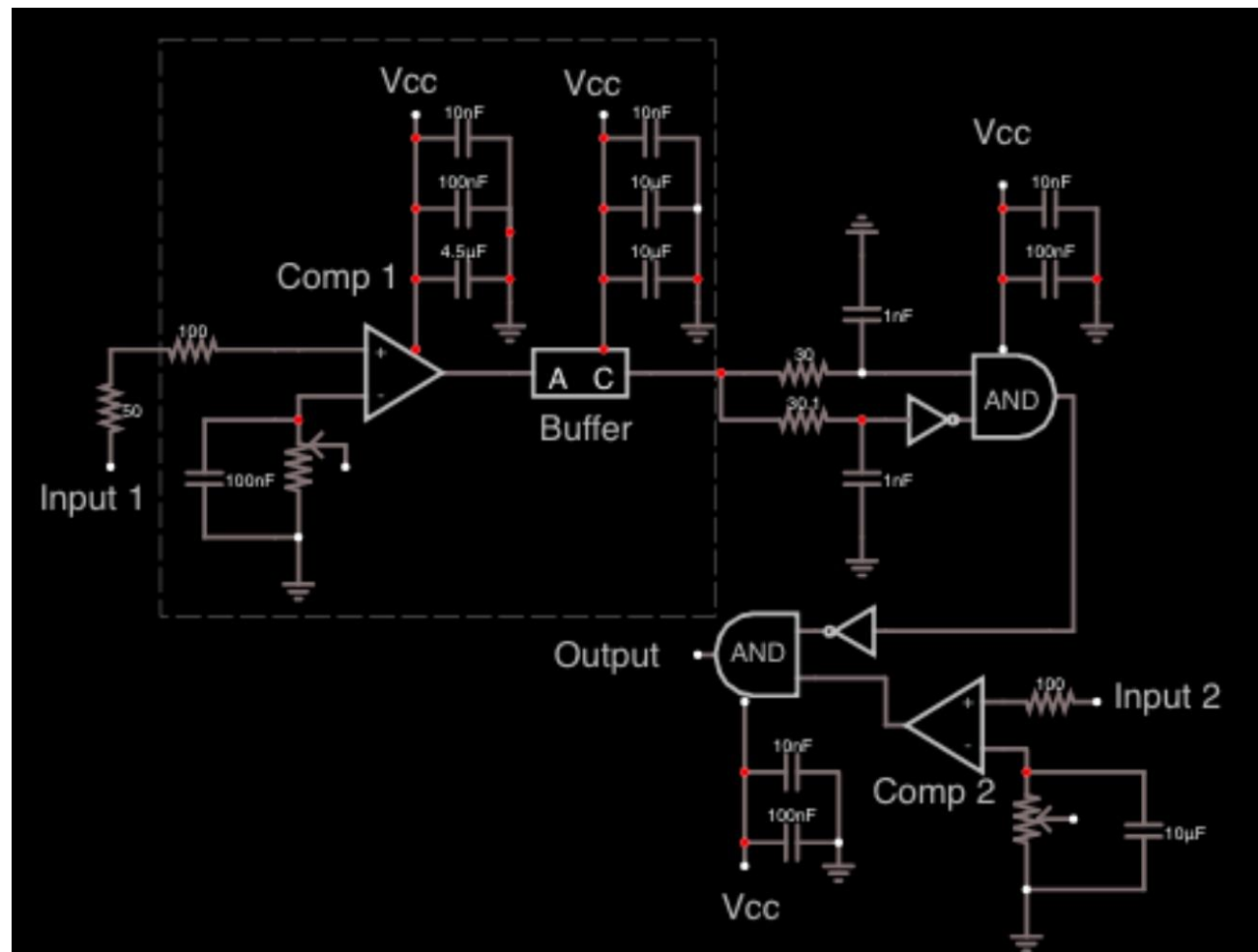


Encountered Problems & Design Modification (Week 5)

 1. New method of delay
2. XOR changed to AND with inverted input
3. NOT added to work with the change from XOR
4. Schmitt Trigger inputs to trigger only on rising edges




Implementing with lab parts

Initial proposed logic

 

 1. DELAY: two BNC cables of different lengths



Time delay created $\Delta t \sim$ Difference in length ΔL

2. XOR gate:

Type	Model	T_{pd} (ns)
NANDS in lab	SNX4LS00	9
XOR in lab	CD4070B	6.8
Purchased XOR	7AC11086	3.8



T_{pd} = Propagation delay in the chip itself, lower bound for rise time: Δt has to be $> T_{pd}$

Summary of prototype results:

Type	Model	T_{pd} (ns)
NANDS in lab	SNX4LS00	9
XORs in lab	CD4070B	6.8
Purchased XORs	7AC11086	3.8

Multiple stages, very slow.
Output of this XOR was noisy,
unable to resolve the Δt delay

  Able to resolve hundreds of ns
pulse width.
Logic worked, but output was not
exactly as desired.




Summary of prototype results:

Type	Model	T_{pd} (ns)
NANDS in lab	SNX4LS00	9
XORs in lab	CD4070B	6.8
Purchased XORs	7AC11086	3.8


Multiple stages, very slow.
Output of this XOR was noisy,
unable to resolve the Δt delay

Able to resolve hundreds of *ns*
pulse width.
Logic worked, but output was not
exactly as desired.

 Clean square-wave output
with $\Delta t = 68\text{ns}$, but
attenuated in amplitude.




x1 attenuation

 

x10 attenuation


Results - Noise Subtraction

 - Made with faster XOR gates
- *Rigol Waveform Generator*: used to simulate the PMT noisy signal to check logic.



Some problems found in slow prototype

 
- The output peaks have 2x frequency than inputs
- Laser TTL's amplitude is too low for gates.
- High frequency bounce and jitter
- Testing
 - Back-reflection distorting the output
 - BNC lengths



Improved design!


Basic logic:

 - Used RC for delay
- AND gates with Schmitt trigger on inputs.




Add ons:

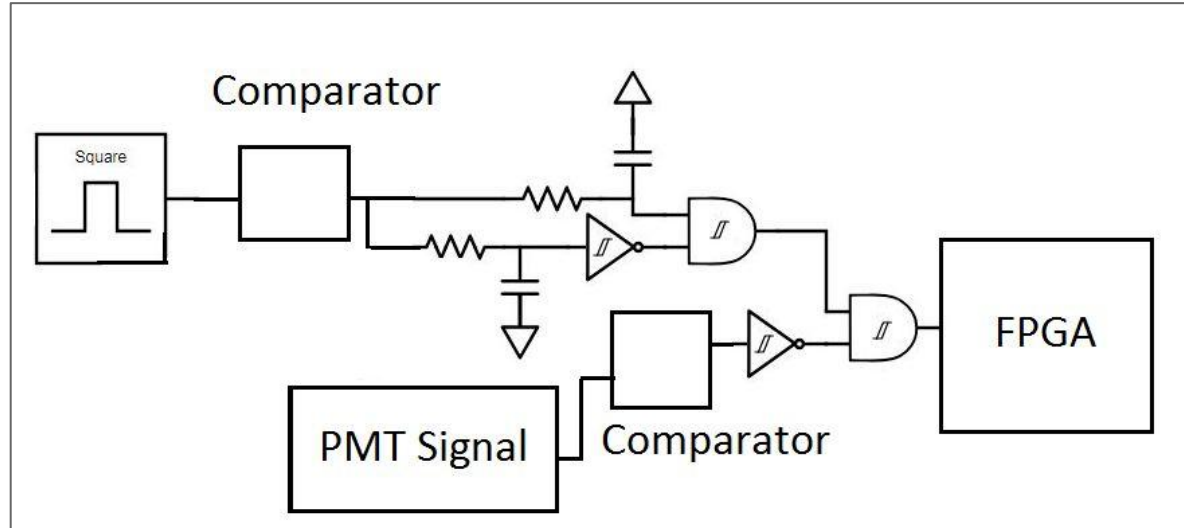- Comparators on inputs
- Decoupling capacitors
- Buffers to clean up the signal.



High speed PCB board design & considerations

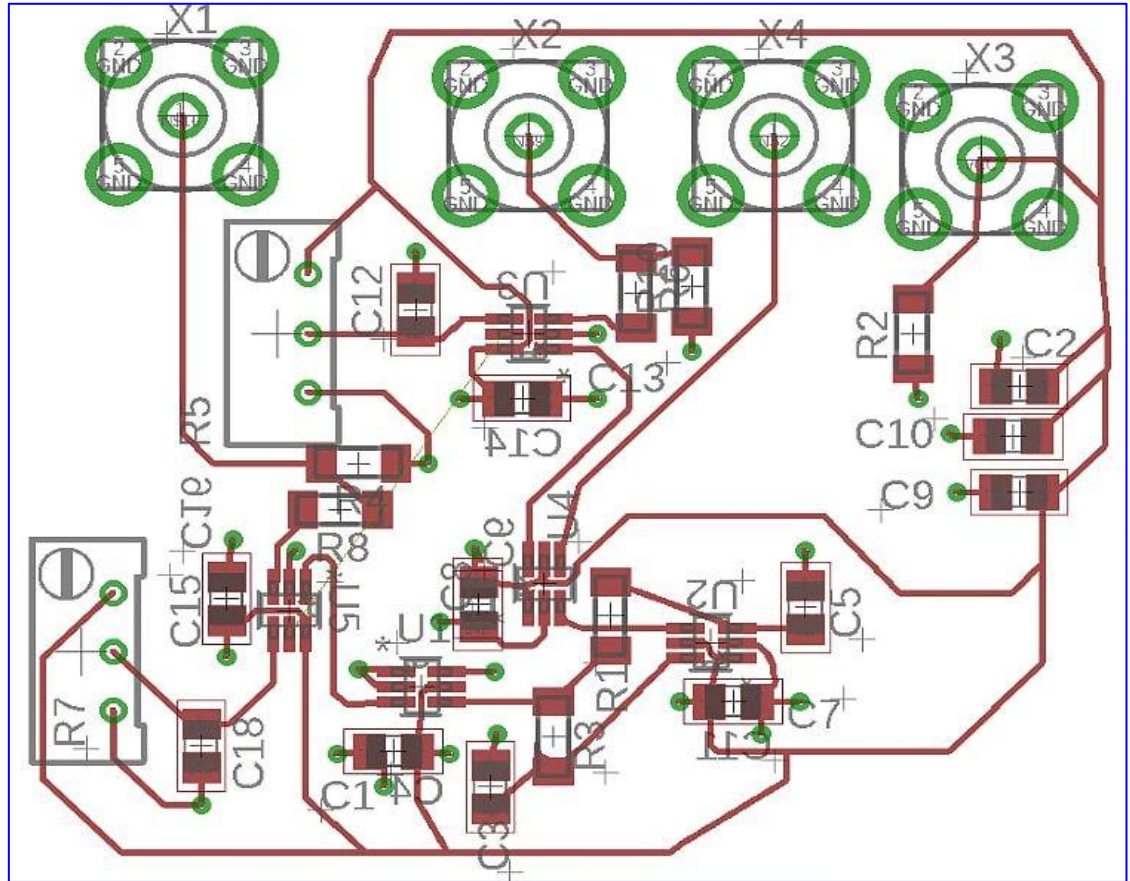- SMAs to replace BNCs
- Various add-on components (capacitors, resistors, buffers, etc.) to ensure signal is nice.
- Followed high-speed PCB board design rules.
- Closely placed components
- Surface mounted parts





Planned	Comments and adjustments
Week 3: Build and test the circuit, basically, have a prototype of a slow version to make sure logic works.	
Week 4: Improve on the prototype to push for as fast as possible. Calculate the timing, rise/fall times, impedance matching for the fast design. Run some simulations of convolution of two functions.	
Week 5: Improve on the design based on prototype. Start and finish implementing the actual design with fast electronics.	<p>We are currently starting to put together the new fast design, it's projected that the circuit board design will take a long time as timing is important.</p> <p>Adjustments:</p> <p>Week 7,8- Finish the complete circuit board design on Eagle, with details of wire lengths, capacitance/resistor values, gate specs, etc., figured out.</p>
Week 6: Testing, debugging and improving.	
Week 7-8: Finalize the product. Test out with ion trap system and obtain actual results.	Week 9: Finalize and test out the board. Write up final report.


Testing the PCB

- Tested each block
- SMAs and adapters
-





Initial proposed concept

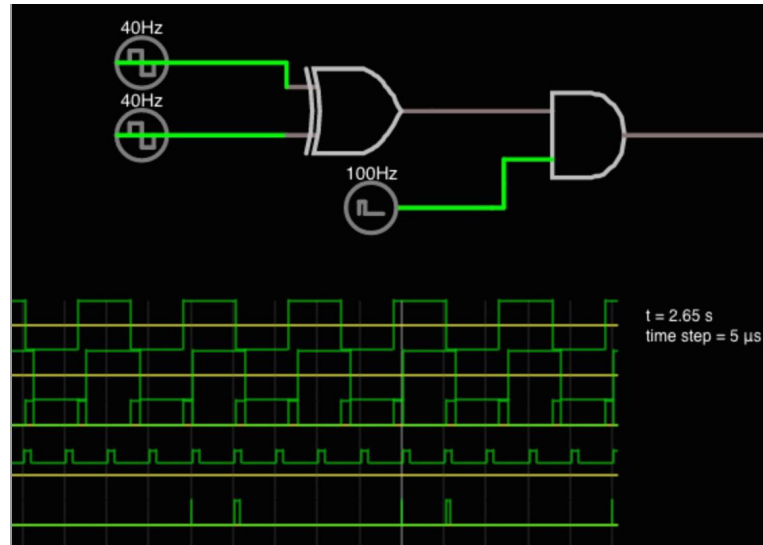 

 


Brief overview of project


Ion trap system (for visualizing)

  


Unwanted spikes from laser pulses

 

Cable length vs time delay

 


Planned	Comments and adjustments
Week 3: Build and test the circuit, basically, have a prototype of a slow version to make sure logic works.	
Week 4: Improve on the prototype to push for as fast as possible. Calculate the timing, rise/fall times, impedance matching for the fast design. Run some simulations of convolution of two functions.	
Week 5: Improve on the design based on prototype. Start and finish implementing the actual design with fast electronics.	We are currently starting to put together the new fast design, it's projected that the circuit board design will take a long time as timing is important. Adjustments: Week 7,8- Finish the complete circuit board design on Eagle, with details of wire lengths, capacitance/resistor values, gate specs, etc., figured out.
Week 6: Testing, debugging and improving.	Week 9: Finalize and test out the board. Write up final report.
Week 7-8: Finalize the product. Test out with ion trap system and obtain actual results.	

 

12.5 ns
10ps


Introduction to the Problem & Objective

 


Objective: Create a sub-nanosecond or picosecond time-resolved “window” to look at the PMT signals, and scan this window in time to reconstruct the cleaner PMT signal.

Some approaches


- Time tagging using time-interval measurements:
 - TDC (time-digital converter)^{3,4}: output the time interval between two events.
 - Ring Oscillator TDC (1-2ps resolution), CMOS TDC (1ps), delay-line based digital TDC...
 - Issue: data storage & retrieval time.
 - Vernier method - the idea of using two clocks of Slightly different periods and the time interval between Them to be measured is expanded by a factor k
- Gating the PMT:
 - Where to gate? Photocathode has rise/fall time.
- Well then... **messing with the PMT output signals!**

 

Proposed design

 


Introduce phase delay

 

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0


Threshold

Some PMT Signal, for example

 

Parts, Planned timeline and Evaluation metric

- HMC721LC3C (14 Gbps, **FAST XOR / XNOR GATE**) - DigiKey
 - Fast rise and Fall times: 19 / 18 ps. Time resolution 14 GHz (70ps)
 - \$150 each

 

Week 3: Build the **circuitry**. Prototype a **slow version** to make sure logic works. Purchase parts.

Week 4: Improve on the **prototype** to push for as fast as possible. Run some **simulations** of convolution of two functions.

Week 5: Improve on the design based on prototype. Start and finish **implementing the actual design** with fast electronics.

Week 6: Testing, debugging and improving.

Week 7-8: Finalize the product. **Test out** with ion trap system and obtain actual results. If time allows, try out TDC.

Week 9 -one of us won't be here (hopefully): Writing up report and working on final presentation.

Evaluation:

- Prototype(s) of slower version and output data. Simulation results. (40% for correct designs of prototype)
- Test results from using the fast autocorrelator on the real experiment. (60% actual implementation)

References

- The Almighty Tony
- Professors Whitehorn and Campbell, who provided invaluable thoughts and advice on possible designs
- Literature (lot of IEEE papers)

[1] Image from *Chapman Labs at Gatech*

[2] Image from “*An Attempt to Calibrate the Laser Induced Fluorescence (LIF) Signal used for Oil Film Thickness (OFT) Measurements in Simulating Test Rigs.*”

[3] Cheng, Zeng, etc. *Recent Developments and Design Challenges of High-Performance Ring Oscillator CMOS Time-to-Digital Converters*. IEEE TRANSACTIONS ON ELECTRON DEVICES, VOL. 63, NO. 1, JANUARY 2016.

[4] Porat, Dan I. *REVIEW OF SUB-NANOSECOND TIME-INTERVAL MEASUREMENTS*.

Introduction to the problem (setup of experiment):

Objective: To make a XOR gate which can perform a desired operation in 12 picoseconds

Methods (two routes, talk a lot about the available ways):

Proposed scheme and design (talk about the planned implementation):

Planned Timeline:

Parts:

Evaluation metric (two prototypes? One actual one with fast electronics and tested out, python simulation): First test with a slower frequency breakdowns using parts that can be found in the lab, we already have a TDC that can take in two inputs, and we can put this together with a XOR gate in the lab. The two inputs for the TDC can be tested using a function generator. As the circuit gets faster, we plan to do a python simulation

